

# CSE 360-Computer Architecture

## Lecture-5

### Internal Memory


Dr. Shamim Akhter

**Computer Science and Engineering**




# Random Access Memory (RAM)

## Volatile Memory

 

- 1) What is the meaning of "Static" and "Dynamic"
- 2) Why is SRAM faster than DRAM?
- 3) Why is DRAM denser than SRAM?
- 4) Structure of SRAM and DRAM

# Semiconductor Memory Cell

 


Three(3) functional terminals carry electrical signal:

- **Select terminal:** selects a memory cell for read and write operation.
- **Control terminal :** indicates **read or write**
- **Data in /out(sense) terminal:**
  - For writing, the Data in terminal provides an electrical signal that sets the state of the cell to 1 or 0.
  - For reading, the data out terminal is used for output of the cell's state.

 
# Static and Dynamic

- SRAM
  - Large array of storage cells (registers)
  - Requires **4-6 transistors per bit**
  - Costly (per bit cost)
  - Holds the stored data as long as power on



Address line

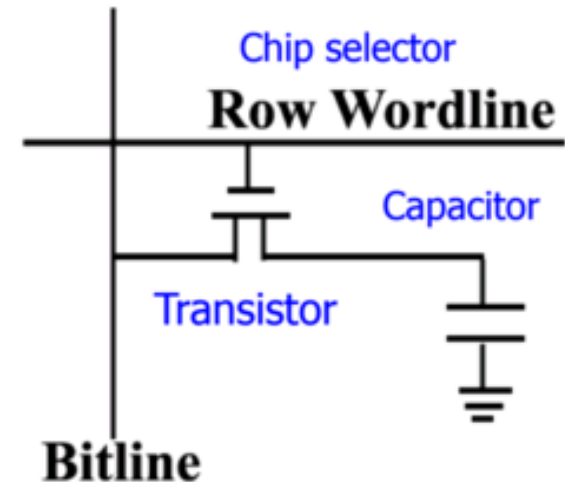- DRAM
  - Requires **1 transistor per bit**
  - Cheaper than SRAM (per bit cost)
  - Density is higher than SRAM
  - Periodically refreshed to prevent loss of stored data




# Reading and Writing with DRAM cell

- Store

- Asserted Wordline
- Bitline 0/1
- Capacitor discharged/charged


- Destructive Read

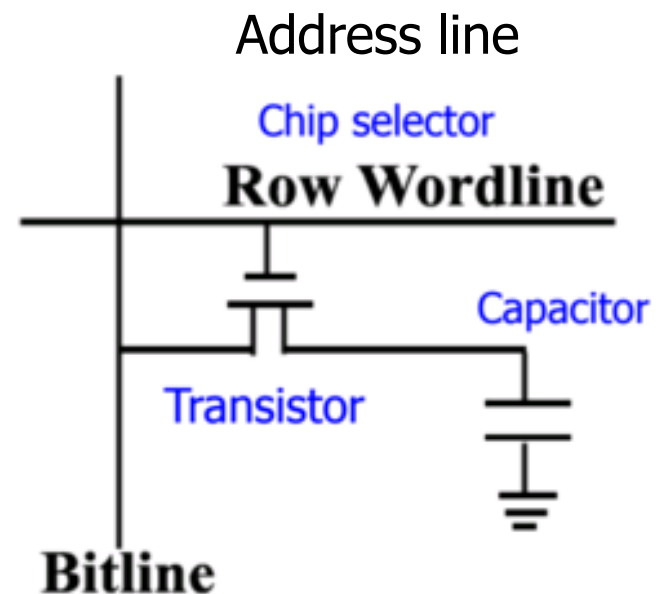- Bitline is precharged to a halfway voltage
- Asserted Wordline
- Bitline voltage is then pulled slightly lower/higher depending on whether the cell stores 0 or 1
- Sense amplifier detects the change and recovers 0/1
- Destructive readout of data must be followed by a write operation to restore the original value.



# Why is SRAM faster than DRAM?

## Why is DRAM denser than SRAM?

 

- Single-transistor memory cell, leads to highest possible storage density
- Reduce per bit cost

Impossible to build a bit stable element with only one transistor

DRAM consists Semi Conducting Transistor Capacitor have a natural tendency to discharge

- leaks a small amount of electricity
- capacitor slowly discharge
- information eventually fades (requires **periodically refreshed**)

# SRAM – Static Random access memory

## Read Operation

Wordline activates T1 and T2 Transistors

If CELL has 1

bitline (BL) is high and bitline(BL') is low

If CELL has 0

bitline (BL) is low and bitline(BL') is high


Sense amplifier senses the two bit lines and sets the corresponding output

## Write Operation

Instead of sensing, drives bit lines (BL and BL')

Appropriate value at BL and its complement in BL'  
and activated word line




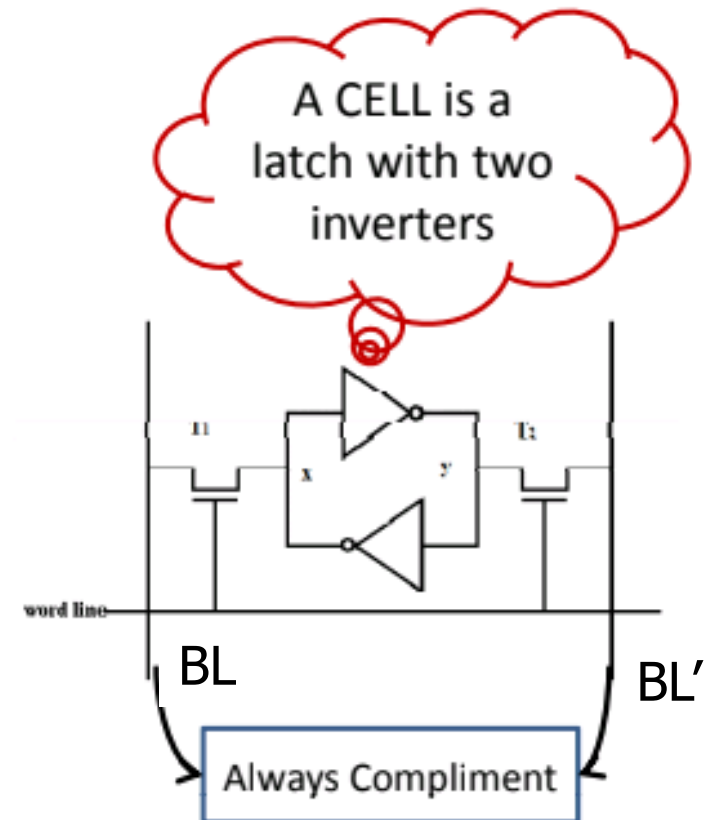
Force the cell to corresponding state and cell retains when the word line is deactivated.



 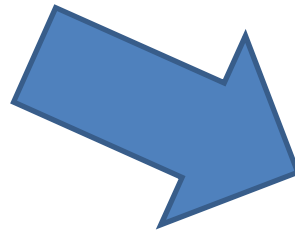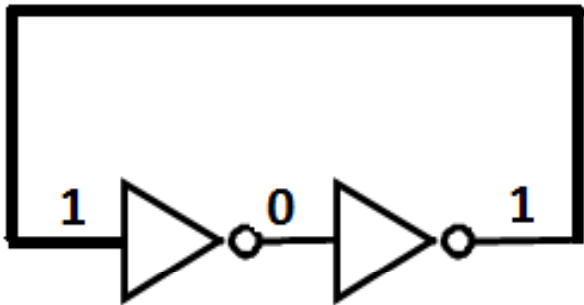
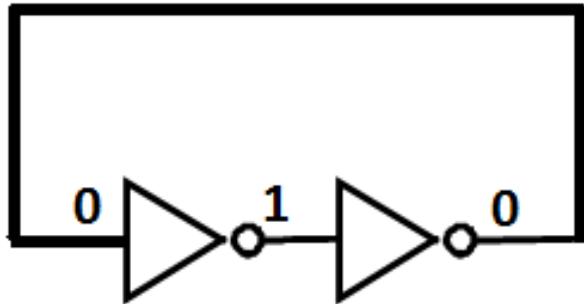
Question: SRAM has 4-6 transistors but we are watching two.  
Where are the others?

- Stable Circuit (same input always same output)

- 1 input  $\rightarrow$  1 output
- 0 input  $\rightarrow$  0 output



  **Storing Capability but Infinite Looping**




**How do we control this circuit??**

**S-R Latch**



# SRAM Cell with Six(6) Transistors

 


Using CMOS Inverters


# Types of ROM

- **Programmable read-only memory (PROM)**
  - Semiconductor memory whose contents are set at once.
  - The writing process is performed electrically and performed by the user **at a time of original chip fabrication**
  - Needs special equipment to program
  - Read “mostly” – read operations are far more frequent than write operations but for which non-volatile storage is required
- **Erasable Programmable (EPROM)**
  - Read and write electrically, as with PROM
  - Before writing, **all storage cells must be erased by ultraviolet (UV) radiation**. [20 minutes take to erase]
  - EPROM is more expensive than PROM but it has advantage of multiple update capability.
- **Electrically Erasable (EEPROM)**
  - Can be written into **anytime without erasing whole contents**; only byte or bytes addressed are updated
  - Takes much longer to write than read
  - EEPROM has advantage of non-volatility with flexibility of being updatable
  - More expensive than EPROM and also less dense (supporting fewer bits per cheap)
- **Flash memory**
  - Erase whole memory or a section (block) electrically within one or a few seconds (in a single action or “**flash**”), which is **much faster than EPROM but slower than EEPROM** but achieves highest density (1 transistor/bit)

# SRAM – Read/Write operation

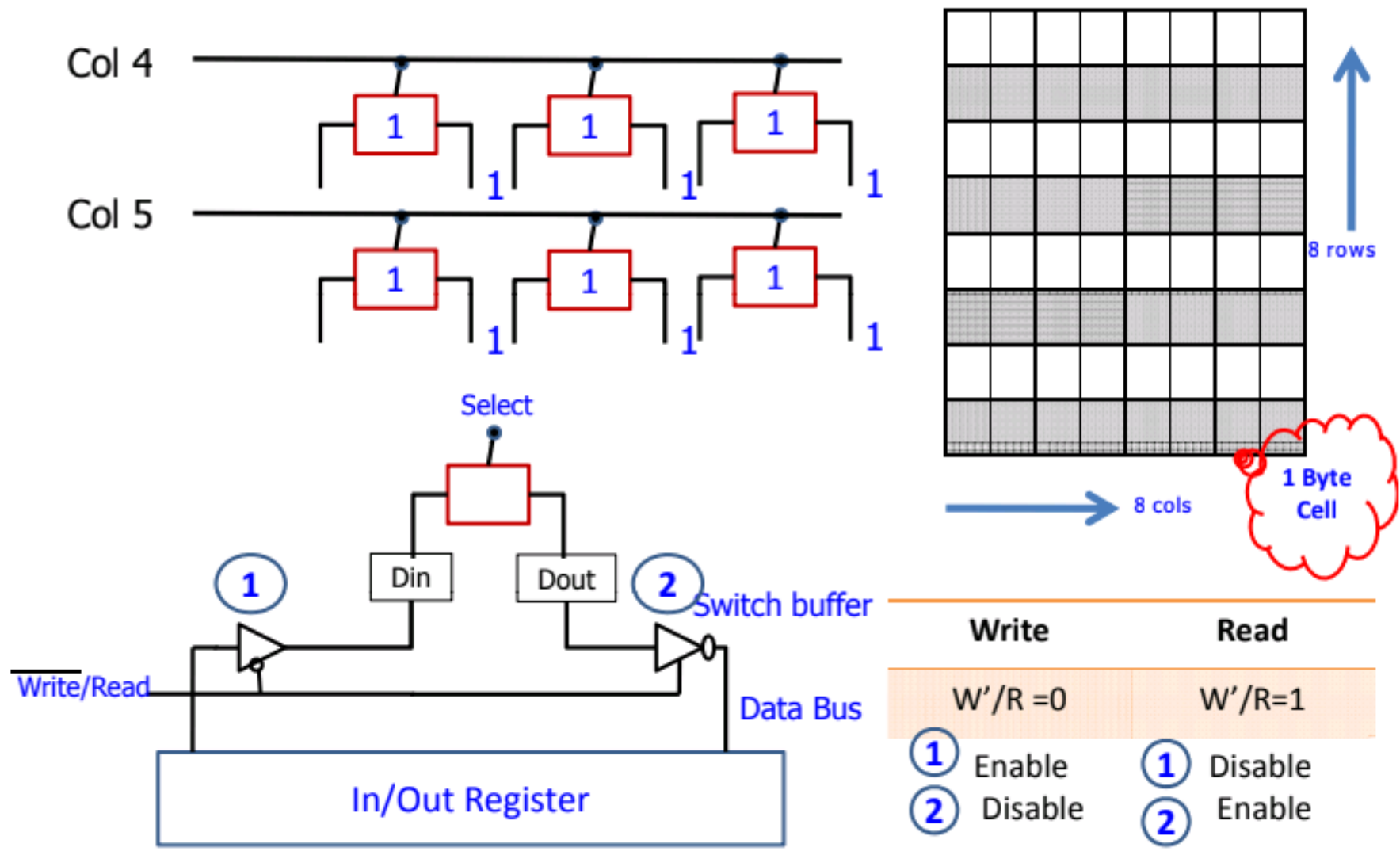

# 32K X 8 RAM

 




$$256 \times 128 = 32768 \text{ cells}$$

$$= 32\text{KB}$$


$$= 32\text{K} \times 8 \text{ bits}$$

$$= 262,144 \text{ bits}$$

# 4k x 1 SRAM

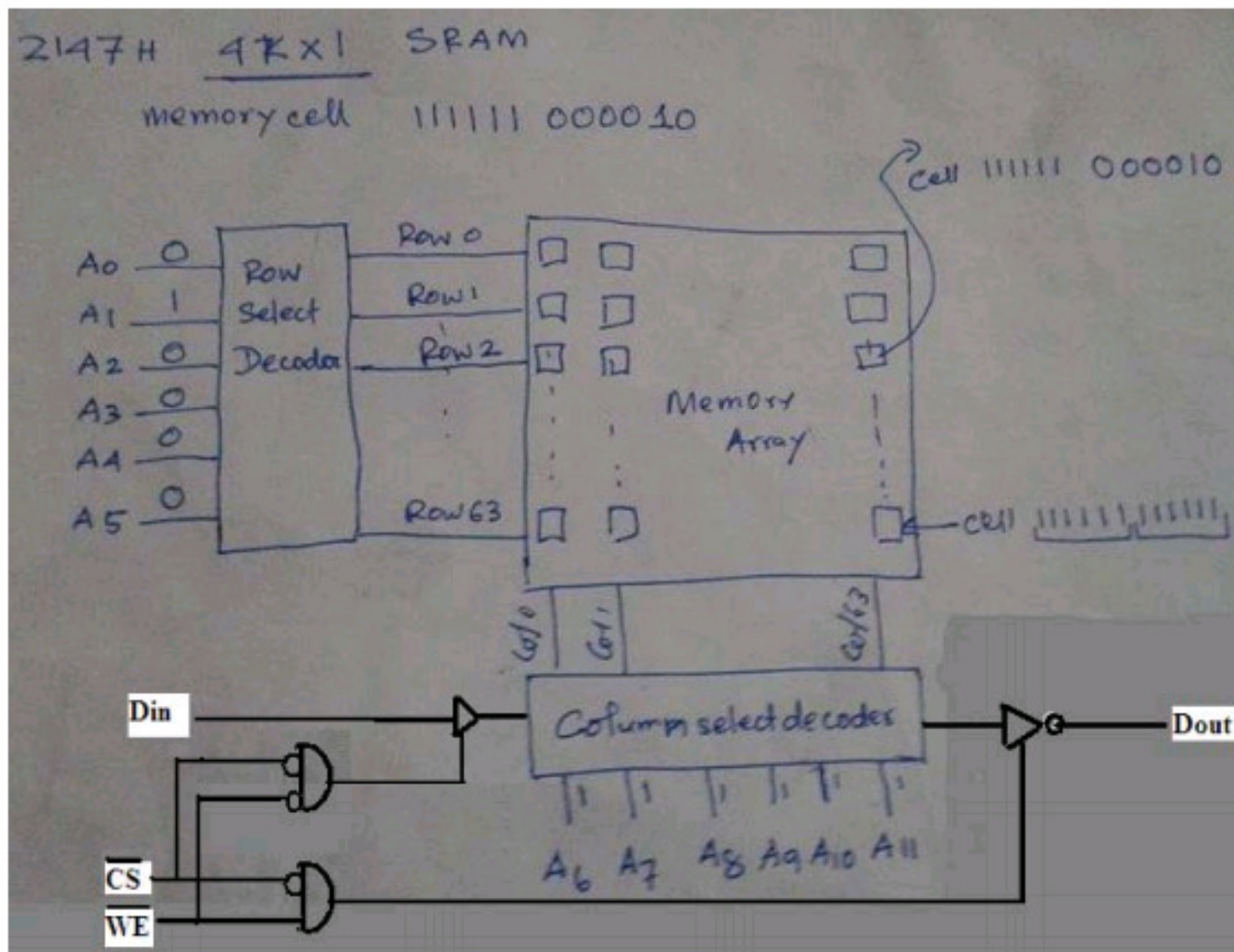  
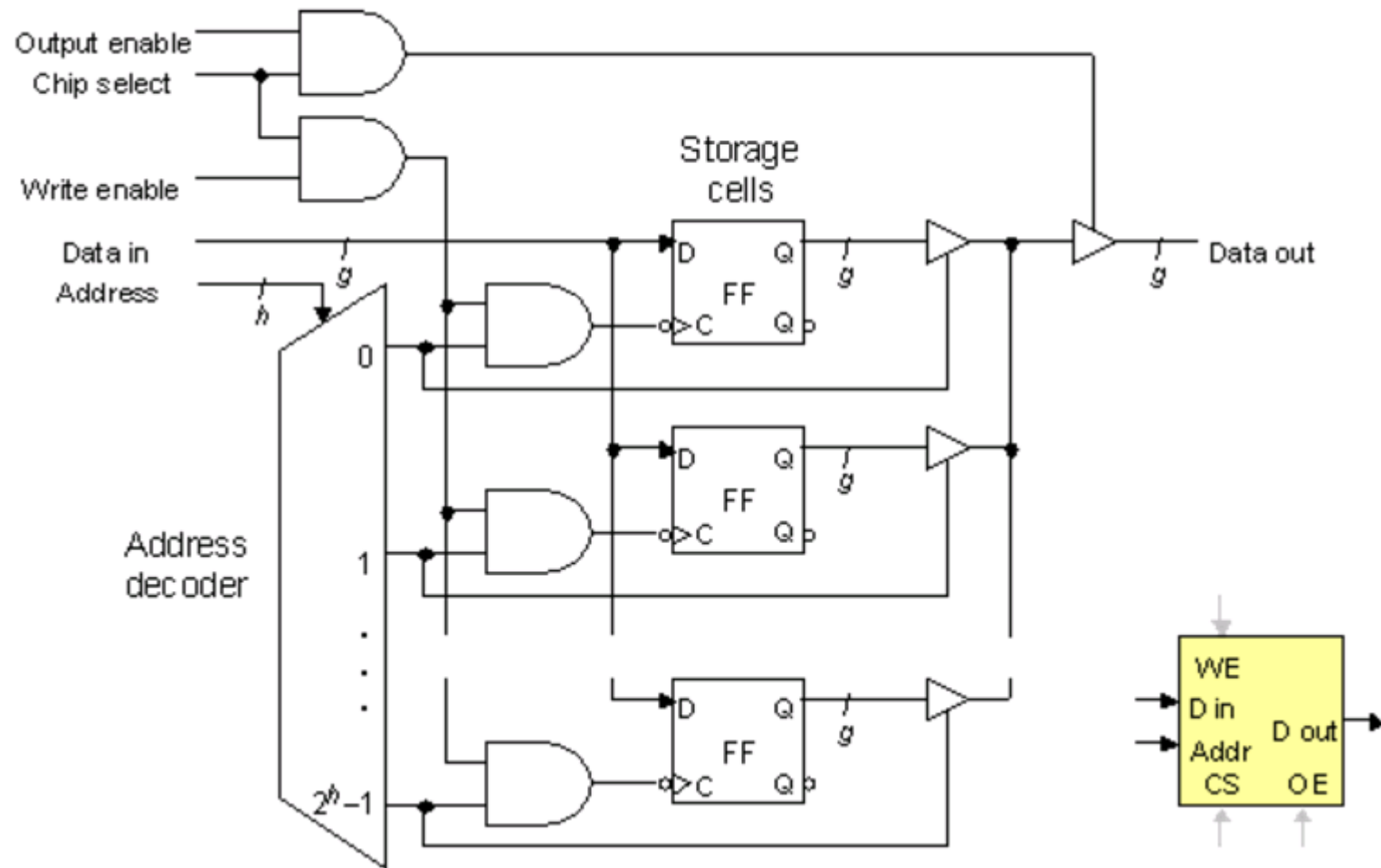
# Conceptual inner structure of a $2^h \times g$ SRAM chip and its shorthand representation



## Multiple-Chip SRAM


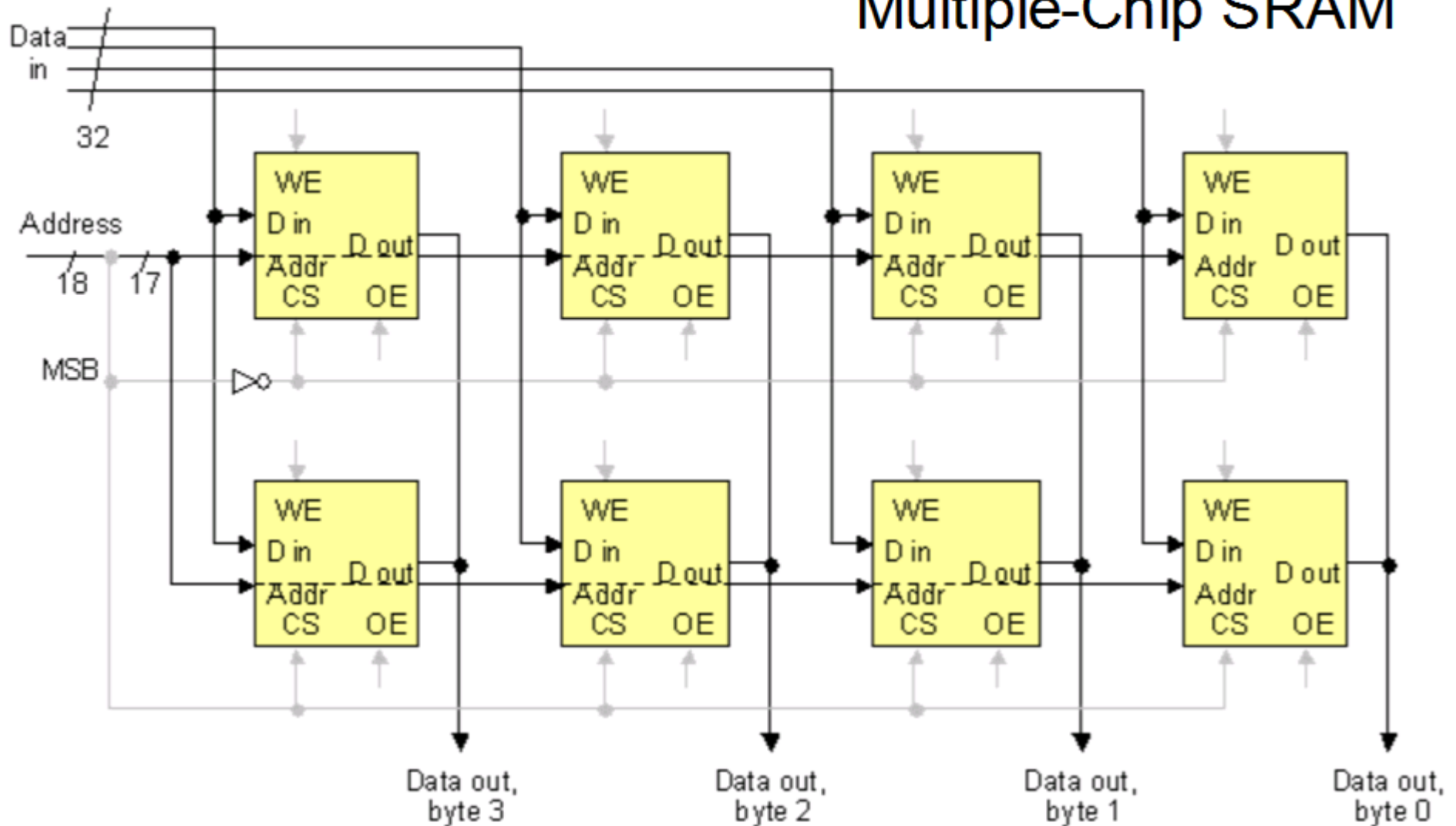


Fig. 17.2 Eight 128K × 8 SRAM chips forming a 256K × 32 memory unit.


# Typical 16 Mb DRAM (4M x 4)

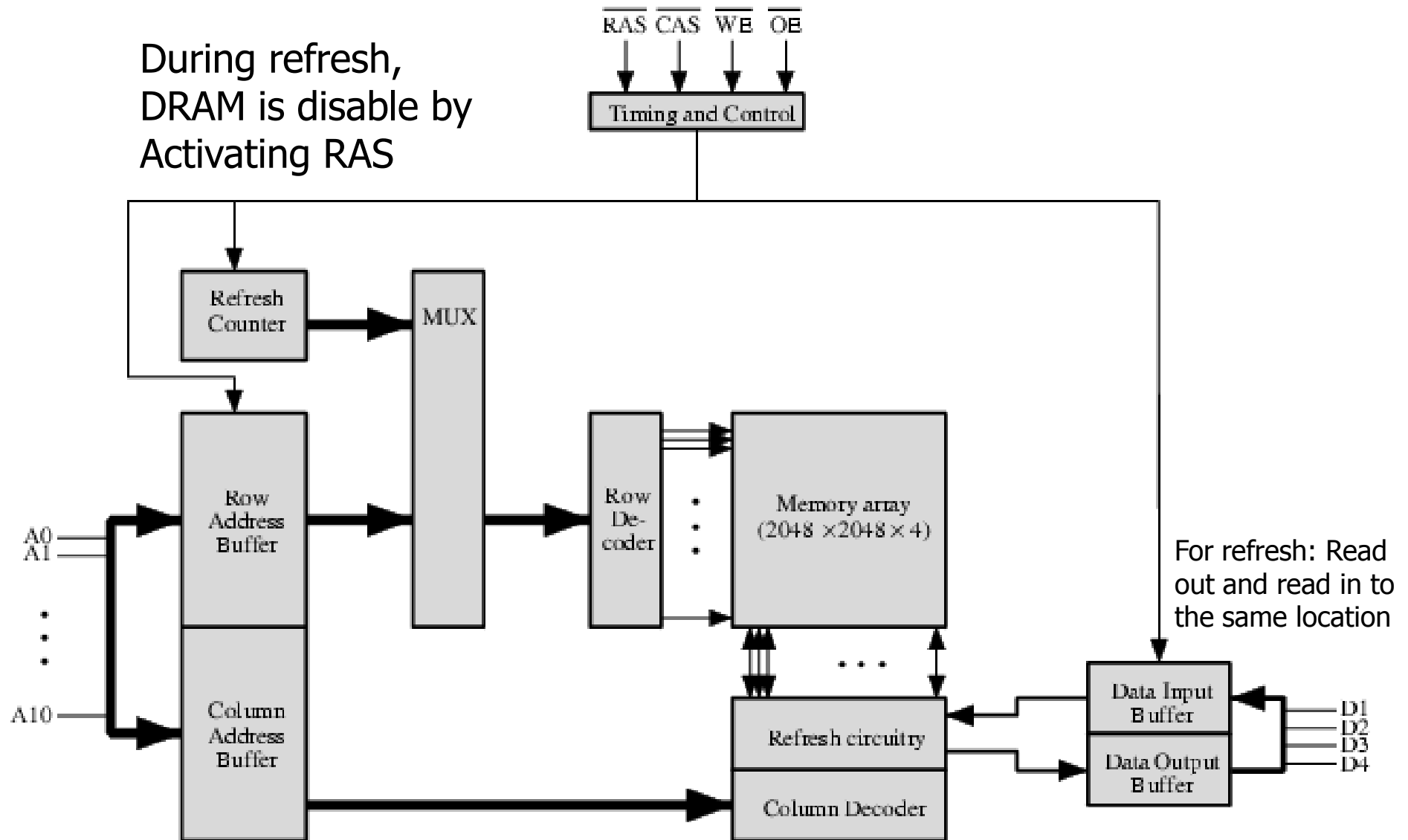


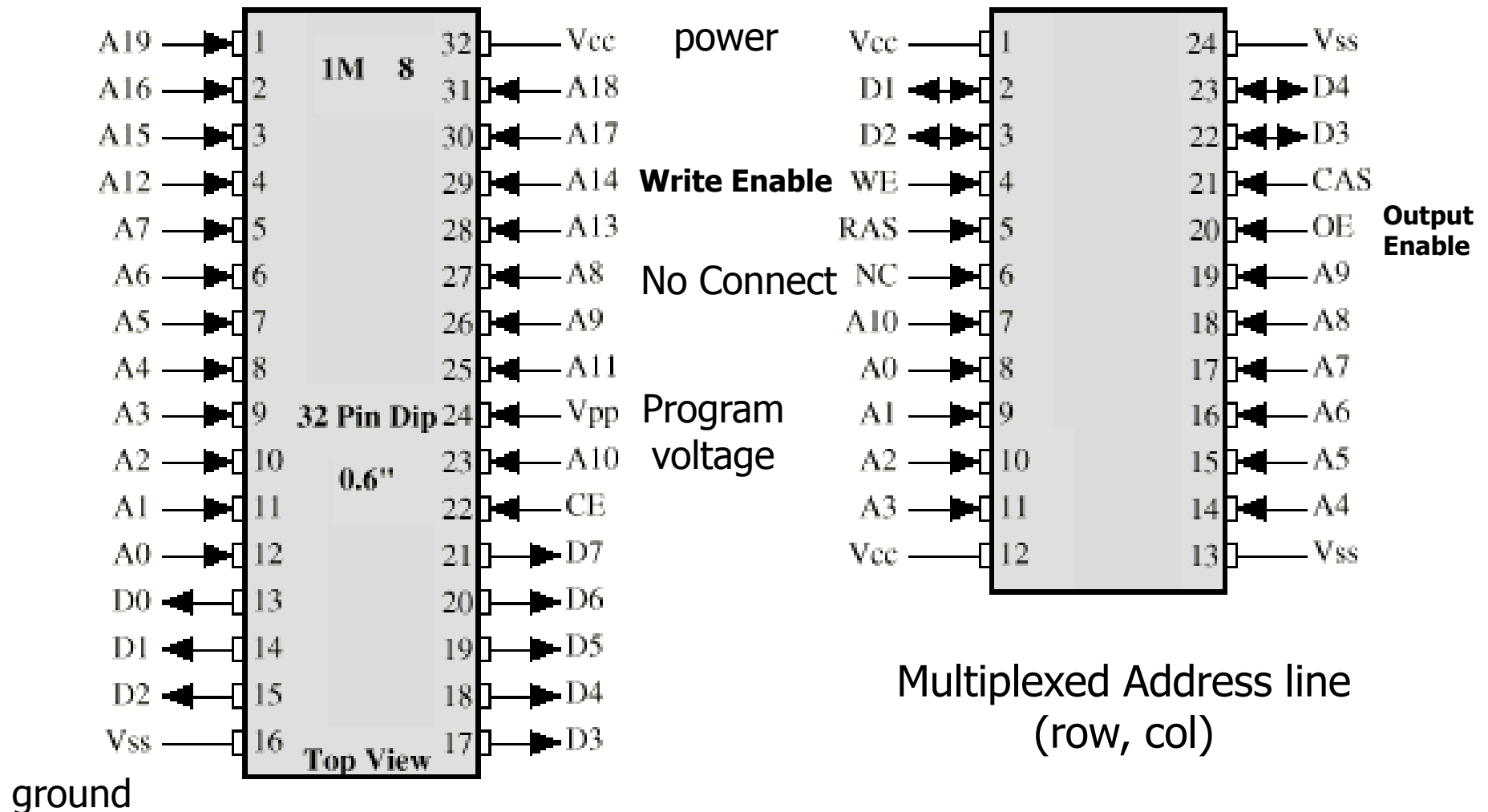
# Chip Packaging- IC

consists pins for connection to the outside world



(a) 8 Mbit EPROM


(b) 16 Mbit DRAM

1Mx 8 bit =  $2^{20}$  x 8 bit

4 M x 4 bits
 
# Pipelined and Interleaved Memory

- Simple memory units -> sequential accesses (one at a time)
- How about memory with multiports?
- How can we increase memory throughput? -> more data can access at once




Pipelined Cache memory/ Memory

Incase memory no tag comparison




Memory Bank

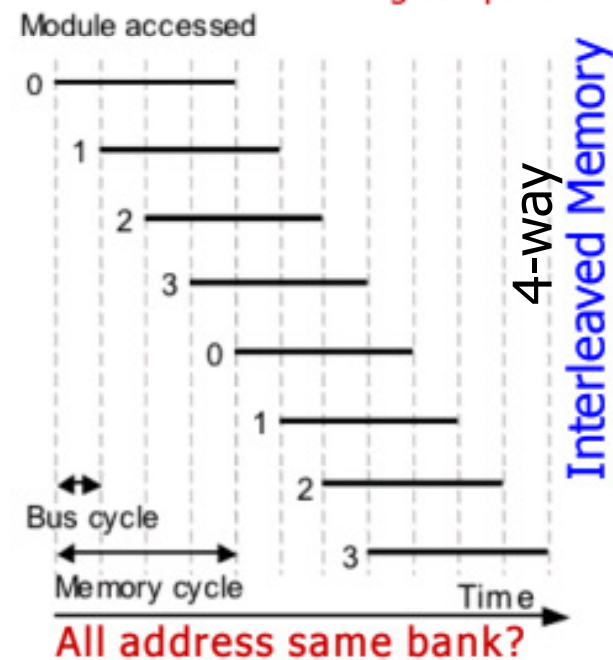

Consecutive words of memory are stored in diff<sup>n</sup> banks, transfer of a block of memory is speed up

# Error Correcting Code Function

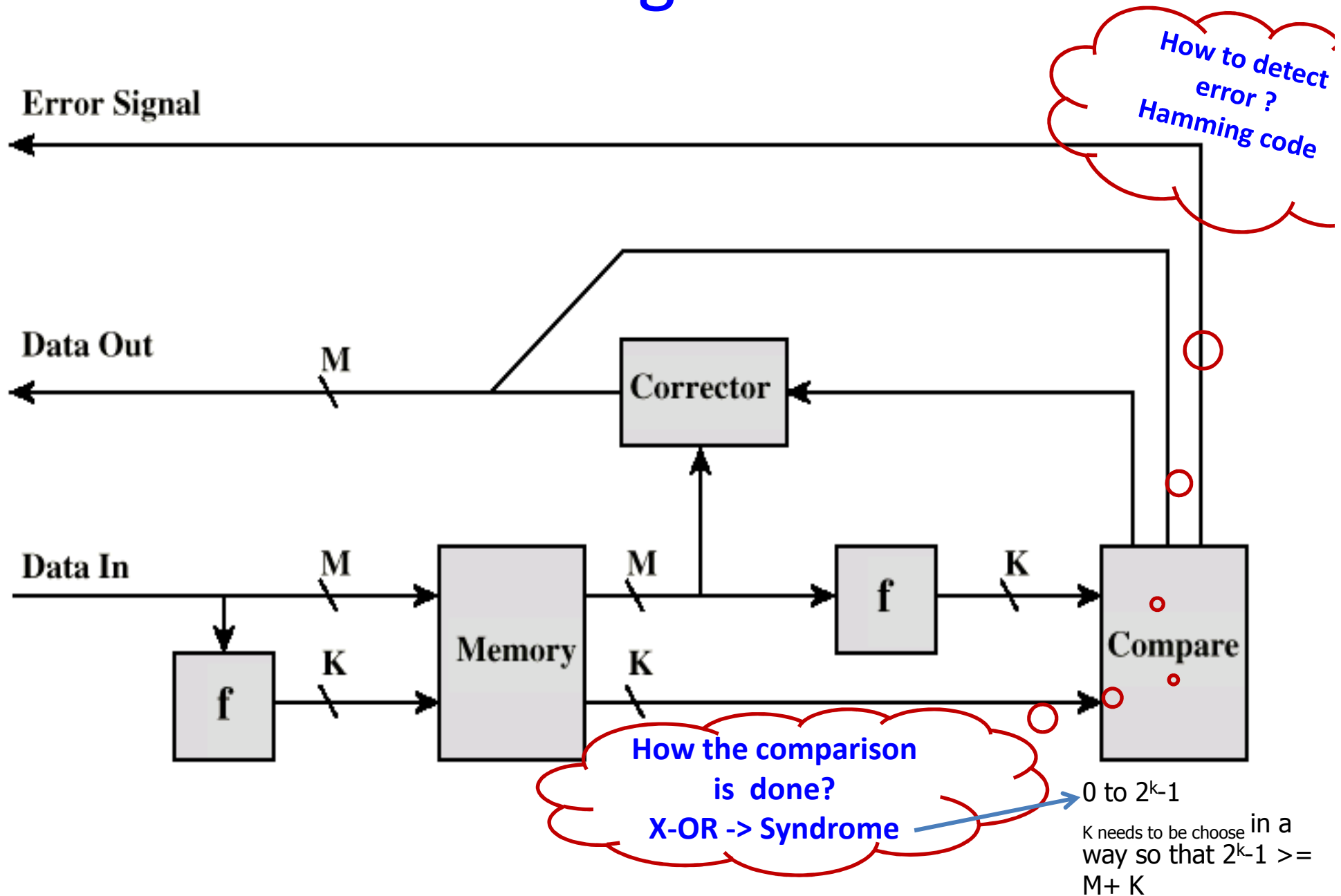


# Hamming Code

## Venn Diagrams

- 4 bits Words ( $M=4$ )
- Choosing Parity bit=1/0
  - so that total # of 1 in circle is **even**

How many  $k$  bits for total  $M$  bit data  
that  $2^k - 1 \geq M + K$

$M$	$K$	
8	3	$2^3 - 1 < M + K$
8	4	$2^4 - 1 \geq M + K$ , 4 bits OK

 

Discrepancies in A and C but not in B

# Layout of Data Bits and Check Bits

Bit Position	12	11	10	9	8	7	6	5	4	3	2	1
Position Number	1100	1011	1010	1001	1000	0111	0110	0101	0100	0011	0010	0001
Data Bit	D8	D7	D6	D5		D4	D3	D2		D1		
Check Bit					C8				C4		C2	C1

# Single-Error-Correcting (SEC) Example

- 8 bits input- 0 0 1 1 1 0 0 1
- Check bits Calculation:
- $C1 = D1 \oplus D2 \oplus D4 \oplus D5 \oplus D7$
- $= 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 1$
- $C2 = D1 \oplus D3 \oplus D4 \oplus D6 \oplus D7$
- $= 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 1$
- $C4 = D2 \oplus D3 \oplus D4 \oplus D8$
- $= 0 \oplus 0 \oplus 1 \oplus 0 = 1$
- $C8 = D5 \oplus D6 \oplus D7 \oplus D8$
- $= 1 \oplus 1 \oplus 0 \oplus 0 = 0$
- $C1=1, C2=1, C4=1, C8=0$

- 8 bits input- 0 0 1 1 1 **1** 0 1
- Check bits Calculation:
- $C1 = D1 \oplus D2 \oplus D4 \oplus D5 \oplus D7$
- $= 1 \oplus 0 \oplus 1 \oplus 1 \oplus 0 = 1$
- $C2 = D1 \oplus D3 \oplus D4 \oplus D6 \oplus D7$
- $= 1 \oplus \mathbf{1} \oplus 1 \oplus 1 \oplus 0 = 0$
- $C4 = D2 \oplus D3 \oplus D4 \oplus D8$
- $= 0 \oplus \mathbf{1} \oplus 1 \oplus 0 = 0$
- $C8 = D5 \oplus D6 \oplus D7 \oplus D8$
- $= 1 \oplus 1 \oplus 0 \oplus 0 = 0$
- $C1=1, C2=0, C4=0, C8=0$

	<b>C8</b>	<b>C4</b>	<b>C2</b>	<b>C1</b>
	0	1	1	1
$\oplus$	0	0	0	1
	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>

6 # bit has error